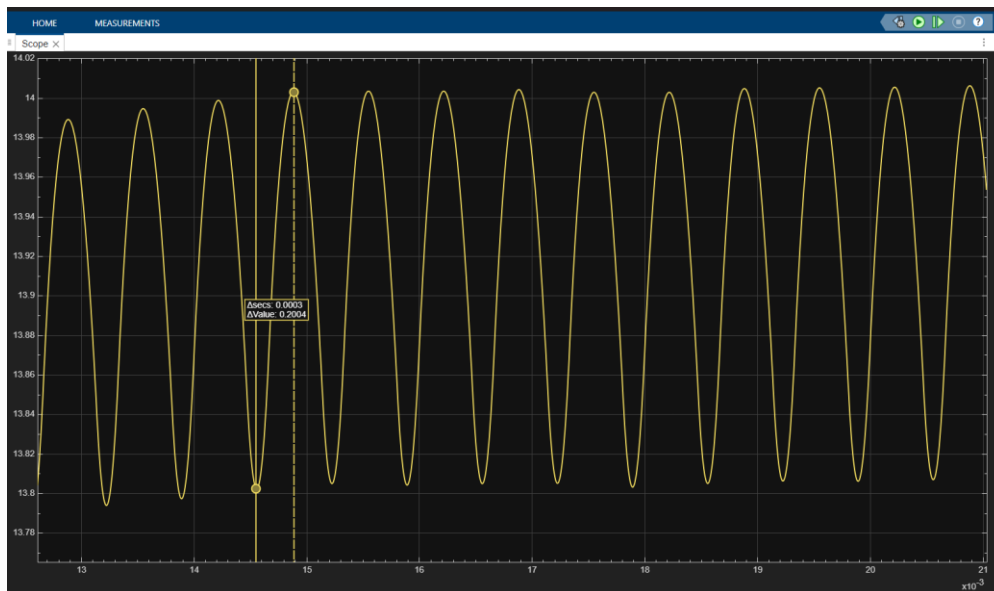


PE project part 2

a)



For output voltage:



My given output voltage ripple: $200 \text{ mV} = 0.2 \text{ V}$

My measured output voltage ripple: 0.2004 V


For coil current:

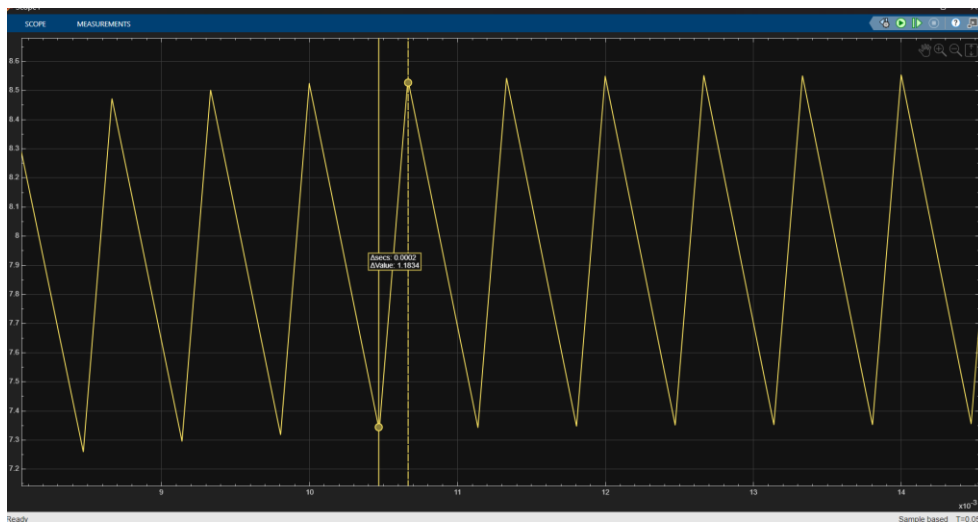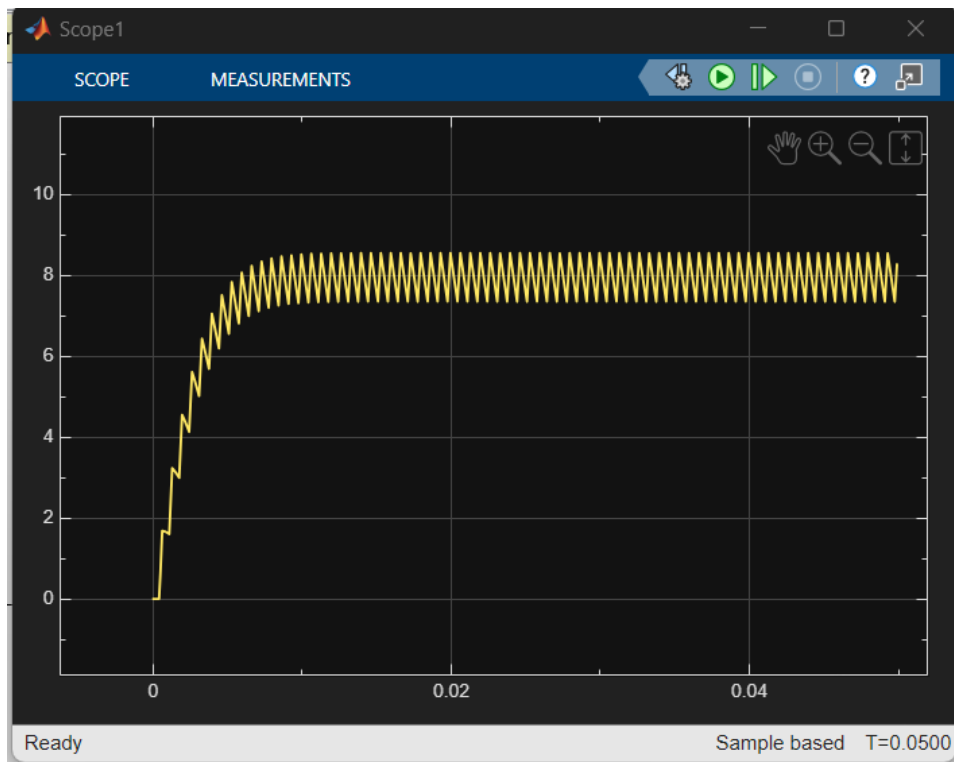

My given coil current ripple: 1.20A


My measured coil current ripple: 1.1834 A

b)

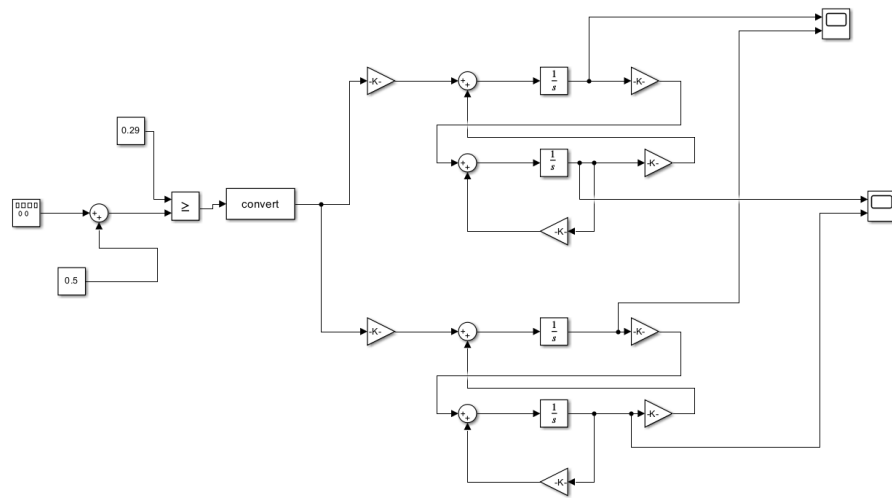

For output voltage:




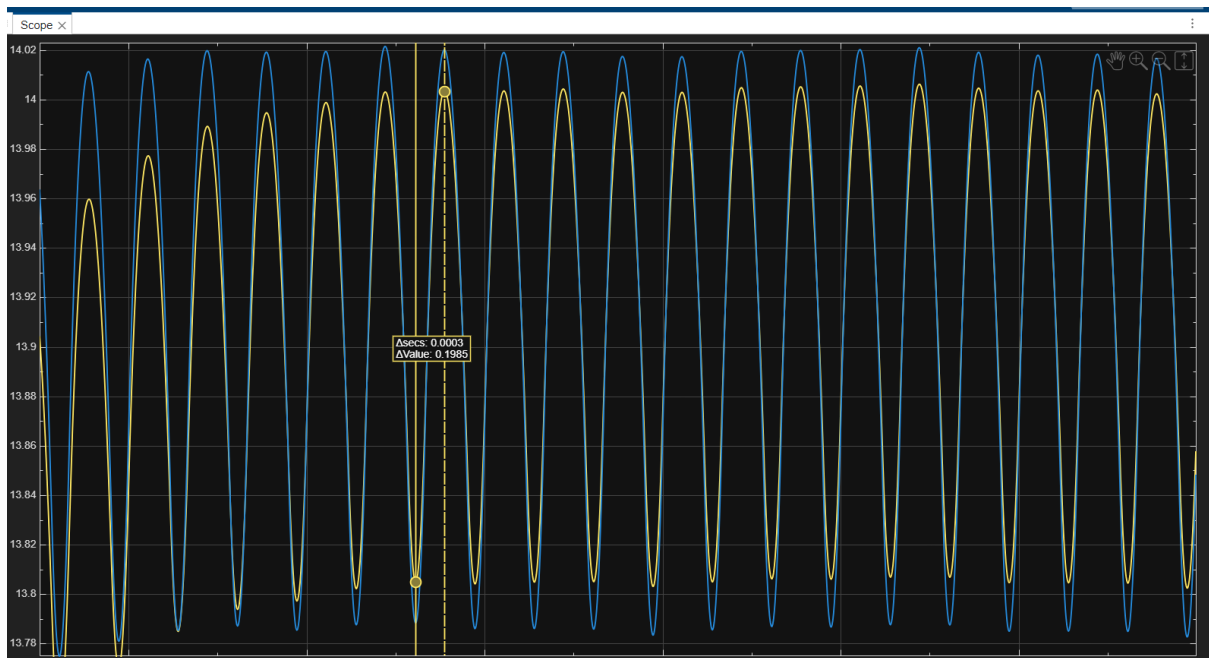

My measured output voltage ripple: 0.2004 V

My output voltage ripple based on datasheet: 0.1985 V



For coil current:

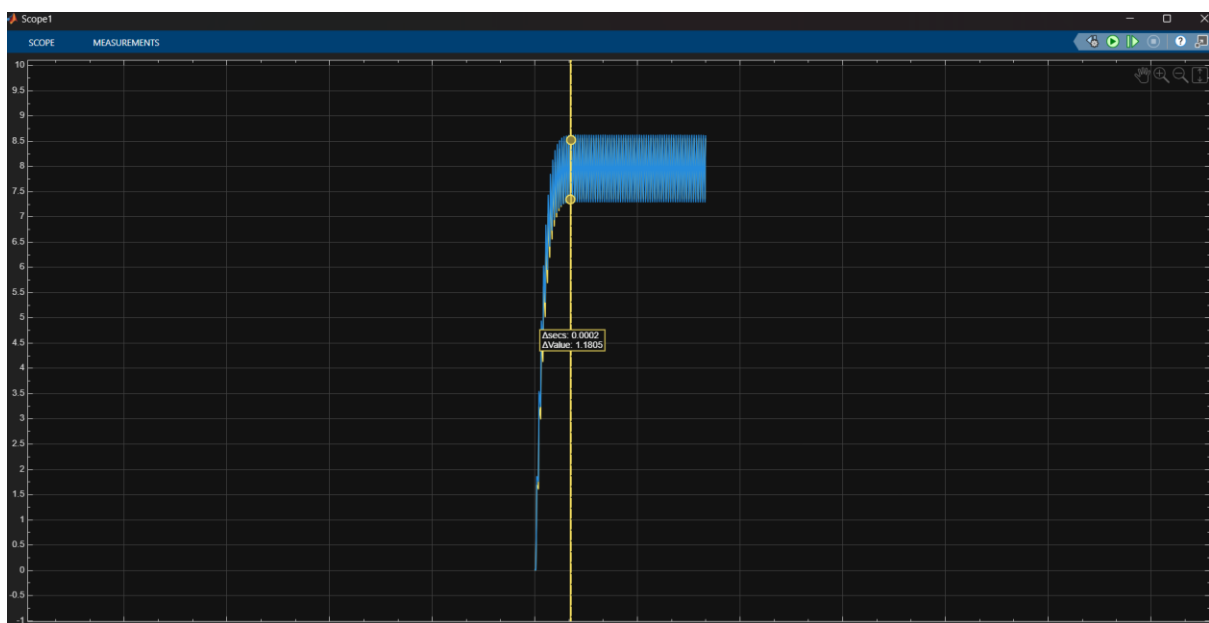


My measured coil current ripple: 1.1834 A

My coil current ripple based on datasheet: 1.1970 A

c)

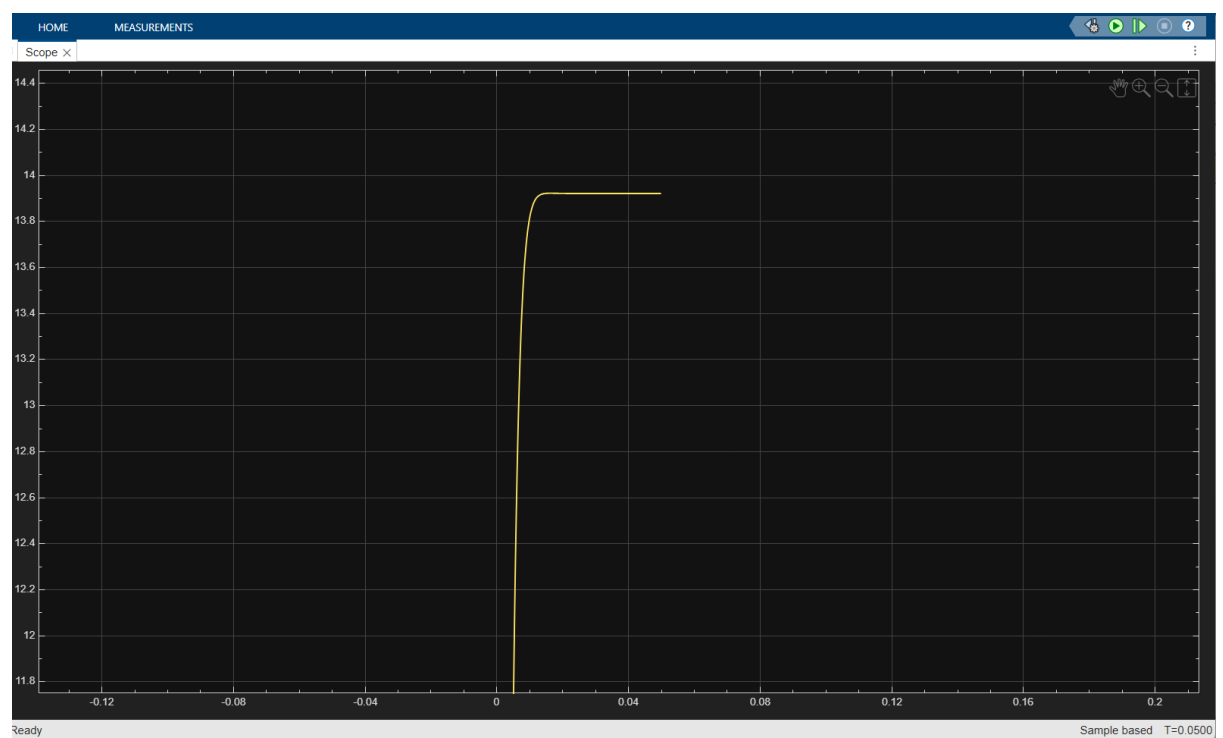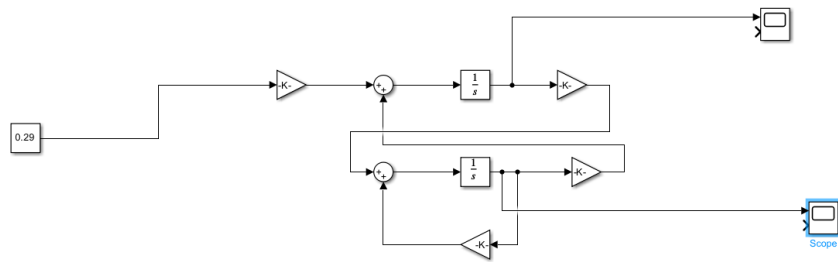

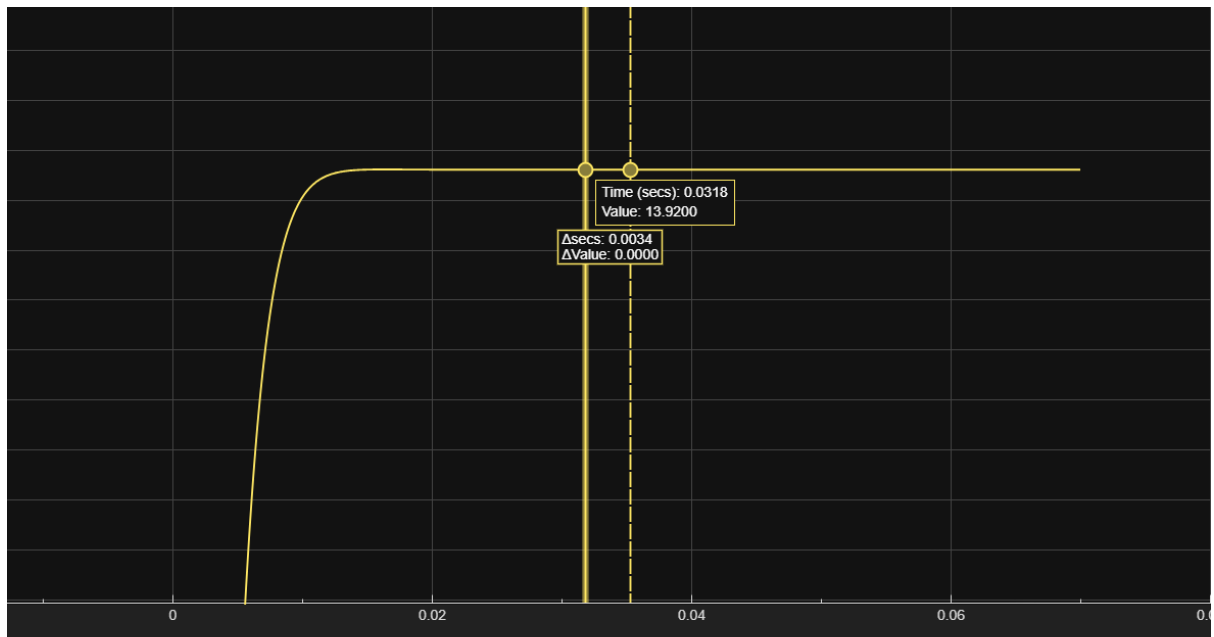

	Max	Peak to Peak
	16.3670 ms	
	13.921207131188691	

Peak value: 13.9212

Steady state value: 13.9200

So overshoot: 0.009% (very small, barely there)

Settling time: 0.025 ms